

OPERATIONAL AMPLIFIERS

Theory and Design

by

Johan Huijsing

Delft University of Technology, The Netherlands

清华大学出版社

北 京

CONTENTS:

SUMMARY	xvii
INTRODUCTION	xix
NOTATION	xxi

1. DEFINITION OF OPERATIONAL AMPLIFIERS ...	1
Nullor Concept.	1
Classification based on number of floating ports	2
1.1 Operational Inverting Amplifier (OIA)	3
Current-to-Voltage Converter	3
1.2 Operational Voltage Amplifier (OVA)	4
Non-inverting Voltage Amplifier	4
Voltage Follower (VF)	5
1.3 Operational Current Amplifier (OCA)	6
Current Amplifier	6
Current Followers (CF)	7
1.4 Operational Floating Amplifier (OFA)	8
Voltage-to-Current Converter	9
Voltage and Current Follower (VCF)	10
1.5 Conclusion	10
1.6 References	12
2. MACROMODELS	15
2.1 Operational Inverting Amplifier (OIA)	15
Definition of: offset voltage and current, input and output impedance, gain	16
2.2 Operational Voltage Amplifier (OVA)	17
Definition of: input bias current, input common-mode rejection ratio	17
2.3 Operational Current Amplifier (OCA)	19
Definition of: output bias current, output common-mode current rejection ratio	19
2.4 Operational Floating Amplifier (OFA)	20

	Using all definitions	21
2.5	Macromodels in Spice	22
	Macromodel mathematical	22
	Macromodel Miller-compensated	23
	Macromodel nested-Miller-compensated	24
	Conclusion	26
2.6	Measurement Techniques for Operational Amplifiers	26
	Gain measurement of an OTA	26
	Gain measurement of an OpAmp	28
	Gain and offset measurements of an OpAmp	29
	General measurement setup for an OpAmp	30
2.7	Problems and Simulation Exercises	33
2.8	References	38

3. APPLICATIONS

3.1	Operational Inverting Amplifier	39
	Current-to-Voltage Converter	40
	Inverting Voltage Amplifier	41
3.2	Operational Voltage Amplifier	42
	Non-Inverting Voltage Amplifier	42
	Voltage Follower	44
	Bridge Instrumentation Amplifier	44
3.3	Operational Current Amplifier	46
	Current Amplifier	46
3.4	Operational Floating Amplifier	48
	Voltage-to-Current Converter	48
	Inverting Current Amplifier	49
	Differential Voltage-to-Current Converter	50
	Instrumentation Voltage Amplifier	52
	Instrumentation Current Amplifier	53
	Gyrator Floating	54
	Conclusion	56
3.5	Dynamic range	56
	Dynamic range over supply-power ratio	56
	Voltage-to-Current Converter	58
	Inverting Voltage Amplifier	59

Non-Inverting Voltage Amplifier	60
Inverting Voltage Integrator	61
Current Mirror	62
Conclusion Current Mirror	63
Non-Ideal Operational Amplifiers	64
Conclusion	66
3.6 Problems	67
3.7 References	72

4. INPUT STAGES	75
4.1 Offset, Bias, and Drift	75
Isolation techniques	76
Balancing techniques	77
4.2 Noise	84
Isolation techniques	84
Balancing techniques	86
Conclusion	88
4.3 Common-Mode Rejection	88
Isolation techniques	89
Balancing techniques	90
Combination of isolation and balancing	90
Common-mode cross-talk ratios (CMCR)	91
Parallel input impedance	92
Collector or drain impedance	94
Tail impedance	95
Collector-base impedance	95
Base impedance	96
Back-gate influence	96
Total CMCR	98
Conclusion	99
4.4 Rail-to-rail Input Stages	100
Constant g_m by constant sum of tail-currents	102
Constant g_m by constant sum of roots of tail currents ..	105
Constant g_m by spill-over control	106
Constant g_m in CMOS by saturation control	112
Constant g_m in CMOS by multiple input stages	114

Constant g_m in CMOS by constant sum of V_{GS}	114
Rail-to-rail in CMOS by back-gate driving	118
Extension of the common-mode input range	118
Conclusion	118
4.5 Problems and Simulation Exercises	119
4.6 References	128
5. OUTPUT STAGES	131
5.1 Power Efficiency of Output Stages	131
5.2 Classification of Output Stages	137
5.3 Feedforward Class-AB Biasing (FFB)	140
FFB Voltage Follower Output Stages	140
FFB Compound Output Stages	146
FFB Rail-to-Rail General-Amplifier Output Stages	149
Conclusion	160
5.4 Feedback Class-AB Biasing (FBB)	161
FBB Voltage-Follower Output Stages	162
FBB Compound Output Stages	163
FBB Rail-to-Rail General Amplifier Output Stages	169
Conclusion	176
5.5 Saturation Protection and Current Limitation	176
Output Saturation Protection Circuits	177
Output Current Limitation Circuits	179
5.6 Problems and Simulation Exercises	183
5.7 References	191
6. OVERALL DESIGN	197
6.1 Classification of Overall Topologies	197
Nine overall Topologies	198
Voltage and current gain boosting	203
Input voltage and current compensation	204
6.2 Frequency Compensation	205
One-GA-Stage Frequency Compensation	207
No internal poles	210
Two-GA-Stage Frequency Compensation	211
Two-GA-stage Parallel Compensation (PC)	212

Two-GA-stage Miller Compensation (MC)	215
Three-GA-Stage Frequency Compensation	224
Three-GA-Stage Nested Miller Compensation (NMC)	225
Three-GA-Stage Multipath Nested Miller Compensation (MNMCM)	228
Four-GA-Stage Frequency Compensation	232
Four-GA-Stage Hybrid Nested Miller Compensation (HNMC)	232
Four-GA-Stage Multipath Hybrid Nested Miller Compensation (MHNMC)	235
Four-GA-Stage conditionally stable MHNMC	237
Multi-GA-Stage compensations	238
Reverse Nested Miller Compensation (RNMC)	238
Conclusion	238
6.3 Slew Rate	239
6.4 Non-Linear Distortion	242
Conclusion	249
6.5 Problems and Simulation Exercises	249
6.6 References	258

7. DESIGN EXAMPLES	261
Nine overall topologies	261
7.1 GA-CF Configuration	262
Operational Transconductance Amplifier (OTA)	262
Folded-Cascode Operational Amplifier	265
Telescopic-Cascode Operational Amplifier	268
Feedforward HF compensation	270
Input voltage compensation	271
Input class-AB boosting	273
Voltage-gain boosting	275
Conclusion	276
7.2 GA-GA Configuration	277
Basic bipolar R-R-out class-A Operational Amplifier	277
Improved basic bipolar R-R-out class-A Operational Amplifier	279
Basic CMOS R-R-out class-A Operational Amplifier	280

	Improved basic CMOS R-R-out class-A Operational Amplifier	281
	Conclusion	282
7.3	GA-CF-VF Configuration	283
	High-Speed bipolar class-AB Operational Amplifier . .	283
	High-slew-rate bipolar class-AB Voltage-Follower Buffer	287
	Conclusion	288
7.4	GA-GA-VF Configuration	288
	General bipolar class-AB Operational Amplifier with Miller Compensation	289
	μ A741 Operational Amplifier with Miller Compensation (MC)	292
	Conclusion	293
7.5	GA-CF-VF/GA Configuration	294
	High-Frequency all-NPN Operational Amplifier with mixed PC and MC	294
	Conclusion	297
7.6	GA-GA-VF/GA Configuration	298
	LM101 class-AB all-NPN Operational Amplifier with MC	298
	NE5534 class-AB Operational Amplifier with bypassed NMC	300
	Precision all-NPN class-AB Operational Amplifier with NMC	302
	Precision HF all-NPN class-AB Operational Amplifier with MNMC	305
	1GHz, all-NPN class-AB Operational Amplifier with MNMC	308
	2Volt Power-efficient all-NPN class-AB Operational Amplifier with MDNMC	308
	Conclusion	310
7.7.	GA-CF-GA Configuration	311
	Compact 1.2Volt R-R-out CMOS class-A OpAmp with MC	311
	Compact 2Volt R-R-out CMOS class-AB OpAmp with	

MC	315
Compact 2Volt R-R-in/out CMOS class-AB OpAmp with MC	318
Compact 1.2Volt R-R-out CMOS class-AB OpAmp with MC	322
Conclusion	324
7.8 GA-GA-GA Configuration	324
1 Volt R-R-out CMOS class-AB OpAmp with MNMC	324
Compact 1.2 Volt R-R-out BiCMOS class-AB OpAmp with MNMC	329
ESD Protection	332
1.8 Volt R-R-in/out bipolar Class-AB OpAmp (NE5234) with NMC	332
Conclusion	337
7.9 GA-GA-GA-GA Configuration	337
1 Volt R-R-in/out Bipolar class-AB OpAmp with MNMC	338
1.2 Volt R-R-out CMOS class-AB OpAmp with MHNMC	344
Conclusion	348
7.10 Problems and Simulation Exercises	348
7.11 References	358

8. FULLY DIFFERENTIAL OPERATIONAL AMPLIFIERS	365
8.1 Fully Differential GA-CF Configuration	365
Fully differential CMOS OpAmp with linear-mode CM-out control	366
Fully differential telescopic CMOS OpAmp with linear-mode CM-out control	368
Fully differential CMOS OpAmp with LTP CM-out control	369
Fully differential GA-CF CMOS OpAmp with input-CM feedback CM-out control	371
Fully differential CMOS OpAmp with R-R buffered resistive CM-out control	372

8.2 Fully Differential GA-CF-GA Configuration	375
Fully differential CMOS OpAmp with R-R resistive CM-out control	375
Conclusion	377
8.3 Fully Differential GA-GA-GA-GA Configuration	378
Fully differential CMOS OpAmp with switched- capacitor CM-out control	378
Conclusion	379
8.4 Problems and Simulation Exercises	380
8.5 References	385

9. OPERATIONAL FLOATING AMPLIFIERS (OFA)	387
9.1 Introduction	387
9.2 Unipolar Voltage-to-Current converter	389
Unipolar single-transistor V-I converter	391
Unipolar OpAmp-gain-boosted accurate V-I converter	392
Unipolar CMOS accurate V-I converter	393
Unipolar bipolar accurate V-I converter	394
Unipolar OpAmp accurate V-I converter	395
Conclusion	396
9.3 Differential Voltage-to-Current converters	396
Differential simple V-I converter	396
Differential accurate V-I converter	397
Differential CMOS accurate V-I converter	398
9.4 Instrumentation Amplifiers	400
Instrumentation Amplifier (semi) with three OpAmps	400
Instrumentation Amplifier with a differential V-I converter for input sensing	401
Instrumentation Amplifier with differential V-I converters for input and output sensing	403
Instrumentation Amplifier with simple differential V-I converters for input and output sensing	404
Instrumentation Amplifier (Bipolar) with common- mode voltage range including negative rail voltage	406
Instrumentation Amplifier CMOS with common-mode	

	voltage range including negative rail voltage	408
	Instrumentation Amplifier simplified diagram and general symbol	409
	Conclusion	410
9.5	Universal class-AB voltage-to-current converter design using an Instrumentation Amplifier	411
	Universal V-I converter design with semi- Instrumentation Amplifier	411
	Universal V-I converter design with real instrumentation amplifier	412
	Conclusion	414
9.6	Universal class-A OFA design	414
	Universal class-A OFA design with floating zener- diode supply	414
	Universal class-A OFA design with supply current followers	415
	Universal class-A OFA design with long-tailed-pairs . .	417
	Conclusion	422
9.7	Universal class-AB OFA realization with power-supply isolation	423
	Universal floating power supply design	424
	Conclusion	424
9.8.	Universal Class-AB OFA design	425
	Universal class-AB OFA design with total-output- supply-current equalization	426
	Universal class-AB OFA design with current mirrors . .	429
	Universal Class-AB OFA design with output-current equalization	430
	Universal class-AB voltage-to-current converter with instrumentation amplifier	432
	Conclusion	433
9.9	Problems	433
9.10	References	439

BIOGRAPHY	443
----------------------------	------------

INDEX	445
--------------------	-----

SUMMARY

A systematic circuit design of operational amplifiers is presented. It is shown that the topology of all operational amplifiers can be divided in nine main overall configurations. These configurations range from one gain stage up to four or more gain stages. Many famous designs are completely evaluated.

High-frequency compensation techniques are presented for all nine configurations. Special focus is on low-power low-voltage architectures with rail-to-rail input and output ranges.

The design of fully differential operational amplifiers and operational floating amplifiers is being developed. Also, the characterization of operational amplifiers by macromodels and error matrices is presented, together with measurement techniques for their parameters.

Problems and simulation exercises have been supplied for self-evaluation.

INTRODUCTION

The goal of this book is to equip the circuit designer with a proper understanding of the theory and design of operational amplifiers (OpAmps). The core of the book presents the systematic design of operational amplifiers. All operational amplifiers can be classified into a periodic system of nine main overall configurations. This division enables the designer to quickly recognise, understand, and choose optimal configurations.

Chapter 1 defines four basic types of operational amplifiers on the basis of the external ground connections of the input and output ports of generalized linear active network elements. Whether an input or output port needs to be isolated from ground has a big impact on the circuit design of the input and output stages, as will be shown in later chapters.

A complete set of linear parameters, by which each of the above four basic types of operational amplifiers can be quantified, is given in Chapter 2. This provides the reader with a sense of which parameters are most important. Chapter 2 also presents macromodels and measurement techniques for OpAmp parameters.

A systematic treatment of sources of errors in important applications of the above four basic types of operational amplifiers is presented in Chapter 3.

Input stages are evaluated in Chapter 4. Important aspects such as bias, offset, noise, and common-mode rejection are considered. Low-voltage input stages with a rail-to-rail input voltage range are extensively discussed.

A classification of push-pull output stages is presented in Chapter 5. Three possible topologies are explored: voltage follower stages, compound stages, and rail-to-rail general amplifier stages. Designs are presented with feedforward and feedback biasing class-AB techniques.

Emphasis is on voltage and current efficiency.

A classification of operational amplifiers into nine main overall configurations is presented in Chapter 6. The classification consists of two two-stage OpAmps, six three-stage OpAmps, and one four- or multi-stage OpAmp. High-frequency compensation techniques are developed for all configurations ranging from one gain stage up to four or more gain stages. Methods are presented for obtaining a maximum bandwidth over power ratio for certain capacitive load conditions. Slew-rate and distortion are also considered.

Chapter 7 presents design examples of each of the nine main configurations. Many well-known OpAmps are fully elaborated. Among them are simple CMOS OpAmps, high-frequency bipolar OpAmps, Precision bipolar and BiCMOS OpAmps, low-voltage CMOS and bipolar OpAmps, and OpAmps with a high output drive capability in CMOS as well as in BiCMOS technology.

The design of fully differential operational amplifiers with common-mode feedback is developed in Chapter 8. Special focus is on low-voltage architectures.

When the output port as well as input port are designed such that they are both isolated from ground, the most universal linear active network element is created: the operational floating amplifier. The concept of this OpAmp gives the designer the freedom to work with current signals as well as voltage signals. Realizations of operational floating amplifiers are developed in Chapter 9 also in relation to instrumentation amplifiers.

Problems and simulation exercises have been supplied for most of the chapters to facilitate self-evaluation of the understanding and design skills of the user of this book.

NOTATION

<i>OpAmp</i>	operational amplifier
<i>OA</i>	operational amplifier
<i>OIA</i>	operational inverting amplifier
<i>OVA</i>	operational voltage amplifier
<i>OCA</i>	operational current amplifier
<i>OFA</i>	operational floating amplifier
<i>GA</i>	general amplifier stage
<i>VF</i>	voltage follower stage
<i>CF</i>	current follower stage
<i>CM</i>	current mirror stage
<i>IA</i>	instrumentation amplifier
<i>a</i>	temperature coefficient
A_v	voltage gain
A_{vo}	DC voltage gain
β	current gain of bipolar transistor
B_v	voltage attenuation of feedback network
<i>C</i>	capacitor value
C_{ox}	specific capacitance of gate oxide
C_M	Miller capacitor value
C_P	parallel capacitor value
<i>D</i>	distortion
<i>f</i>	frequency
f_T	transit frequency of a transistor
f_o	zero-dB frequency
g_m	transconductance of a transistor
<i>i</i>	small-signal current
<i>I</i>	current
I_B	bias current
I_C	collector current
I_D	drain current
I_E	emitter current
I_S	supply current
I_Q	quiescent current

k	Boltzman's Constant
K	$= \mu C_{ox} W/L$
L	length of gate in MOS transistors
M	CMOS transistor
R	resistor value
S	signal
S_r	slew rate
T	generalized transistor
Q	bipolar transistor
v	small-signal voltage
V	voltage
V_B	bias voltage
V_{CC}	positive supply voltage with bipolar transistors
V_{DD}	positive supply voltage with MOS transistors
V_{EE}	negative supply voltage with bipolar transistors
V_G	generator voltage
V_{GS}	gate-source voltage
V_{GT}	active gate-source voltage ($V_{GS} - V_{TH}$)
V_S	total-supply voltage
V_{SN}	negative supply voltage
V_{SP}	positive supply voltage
V_{SS}	negative supply voltage with MOS transistors
V_T	thermal voltage kT/q
V_{TH}	threshold voltage of MOS device
W	width of gate in MOS transistors
μ	mobility of charge carriers

Extrinsic device parameters

R_L
 C_L
 C_M
 $R_D R_C$
 $R_G R_B$
 $R_S R_E$

Intrinsic Small-signal transistor parameters r_{ds} r_{ce} r_o r_{gs} r_{be} r_s r_e C_{ds} C_{ce} C_{gs} C_{be} g_m g_m μ_n μ_p β_n β_p

1. DEFINITION OF OPERATIONAL AMPLIFIERS

Nullor Concept

In 1954 Tellegen introduced the concept of a universal active network element under the name of "ideal amplifier" [1.1]. The name "nullor", generally accepted now, was given to it by Carlin in 1964 [1.2]. The symbol of a nullor is shown in Fig. 1.1.

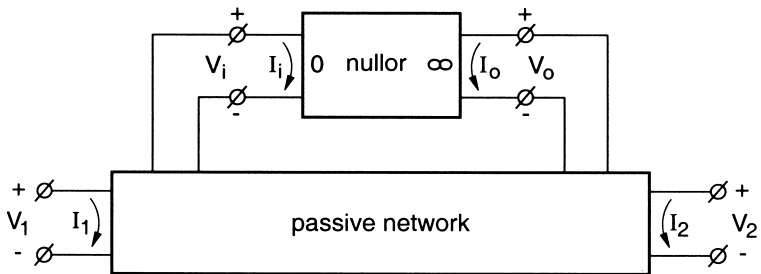


Fig. 1.1: A two-port network composed of a passive network and a nullor

The nullor is defined as a two-port network element whose ports are called input and output ports and whose input voltage V_i and input current I_i are both zero, so:

$$\begin{aligned} V_i &= 0, \\ I_i &= 0 \end{aligned} \quad (1.1)$$

The nullor concept only has significance if a passive network external to the nullor provides for a feedback from the output port into the input port [1.3]. The output voltage V_o and the output current I_o will be determined by the passive network elements in such a way that the input requirements $V_i=0$, $I_i=0$ are satisfied.

An accurate signal transfer requires, firstly, accurate passive components and secondly, a practical nullor realization which approximates $V_i=0$, $I_i=0$.

This implies that the nullor realization should have a high gain, a low input noise, and low offset voltage and current (see Chap. 2.1). All linear and non-linear analog transfer functions can be implemented with nullor realizations and passive components.

Classification based on number of floating ports

We will now classify four nullor types on the basis of the number of ports which are floating, beginning with both ports grounded and ending with both ports floating. There are two main reasons for this kind of classification. Firstly, the larger the number of ports which are grounded the simpler the construction of the active device will be. Secondly, the larger the number of grounded ports the lower the number of possible feedback topologies will be allowed.

We will give each of the four nullor types a name which will be explained later. The first one with two grounded ports will be called operational inverting amplifier (OIA). The second one with the input port floating and output port grounded will be called operational voltage amplifier (OVA). The third one with the input port grounded and output port floating will be called operational current amplifier (OCA). Finally, the fourth one with both ports floating will be called operational floating amplifier (OFA). The adjective "operational" was coined by John R. Ragazzini and his colleagues in a paper [1.4] published in 1947. That paper described the basic properties of an OIA used with linear and nonlinear feedback. The adjectives "inverting" (I), "voltage" (V), "current" (C), or "floating" (F), are given by the present author to distinguish the four types of Operational Amplifiers according to their most striking attribute, as we will see in the next sections of this chapter. The most popular one, the OVA will be shortened to OpAmp in most parts of this book, where the distinction between the different types is not needed.

1.1 Operational Inverting Amplifier (OIA)

A practical approximation of a nullor having both ports grounded will be called an "operational inverting amplifier" (OIA). The grounded input port makes the construction of the input stage relatively easy, because it only needs to function at one voltage level [1.4] [1.5]. Similarly, the grounded output port makes it relatively easy to construct an output stage having a high power efficiency, because the current return path can be directly connected to the grounded supply voltages. The negative sign (inverting) of the amplification factor makes it possible to obtain stable negative feedback with passive components connected directly from the output to the input port. The parallel connection of the feedback circuit at the input and output of the amplifier results in a low virtual entrance impedance (see Chap. 3.1), suitable for accurate current sensing at virtual zero input power, and a low exit impedance, suitable for obtaining an accurate output voltage.

Current-to-Voltage Converter

The most simple application of an OIA is the transimpedance amplifier or current-to-voltage transactor. This circuit is shown in Fig. 1.1.1.a with a symbol of a nullor and in Fig. 1.1.1.b with a practical symbol of an OIA.

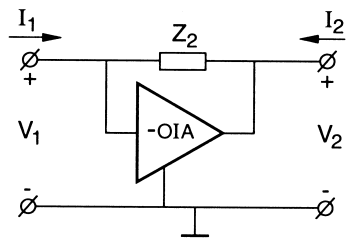
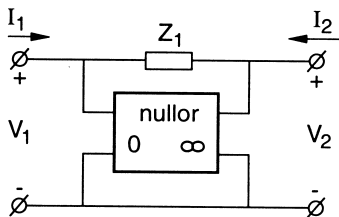


Fig. 1.1.1.a: Transimpedance amplifier with a nullor symbol

Fig. 1.1.1.b: Transimpedance amplifier with an OIA symbol

The current-to-voltage transfer factor

$$Z_t = V_2/I_1 = -Z_1, \text{ at } V_1 = 0 \quad (1.1.1)$$

can be accurately determined by $-Z_1$ if the OIA satisfies two requirements: firstly, a high gain, and secondly, a low input offset voltage and offset current. A high gain also assures low entrance and exit impedances.

1.2 Operational Voltage Amplifier (OVA)

A practical nullor approach having only the output port grounded and the input port floating [1.6, 1.7] will be called "operational voltage amplifier" (OVA) or OpAmp. Currently, it is the most widely applied universal active device. The floating character of the input port imposes special demands on the construction of the input circuit, as will be discussed in Chapter 4.3 and 4.4. The floating input port allows series coupling of negative feedback.

This results in a high entrance impedance suitable for accurate voltage sensing at virtual zero input power. The parallel coupling of the feedback network with the grounded output port assures a low exit impedance.

Non-inverting Voltage Amplifier

The most essential application of the OVA is the non-inverting voltage amplifier or voltage-to-voltage transactor. The circuit is drawn in Fig. 1.2.1.a with a nullor symbol and in Fig. 1.2.1.b with a practical amplifier symbol for an OVA.

The voltage amplification factor

$$A_u = V_2/V_1 = (Z_1 + Z_2)/Z_2, \text{ at } I_1 = 0 \quad (1.2.1)$$

can be accurately determined by the impedance ratio $(Z_1 + Z_2)/Z_2$ if the OVA satisfies the requirements: a high gain, a low input offset voltage and current, independent of the common-mode voltage of the input port,

and a low input bias current. A high gain assures a high entrance impedance and a low exit impedance.

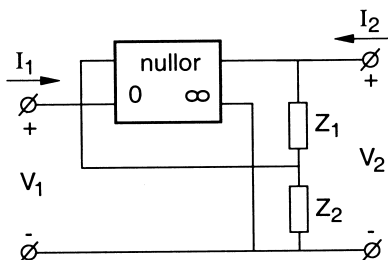


Fig. 1.2.1.a: Voltage amplifier with a nullor symbol

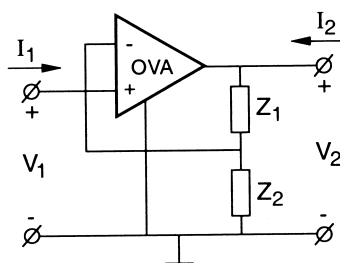


Fig. 1.2.1.b: Voltage amplifier with an OVA symbol

Voltage Follower (VF)

A special situation occurs if the OVA has its negative input terminal connected with the output terminal. We will call such a device a "voltage follower" (VF), because the exit voltage follows the entrance voltage. The construction of a universal active device with this connection may be simpler than without this connection, because no voltage shifting is required between the input and output. The VF circuit is given in Fig. 1.2.2.b with an OVA symbol.

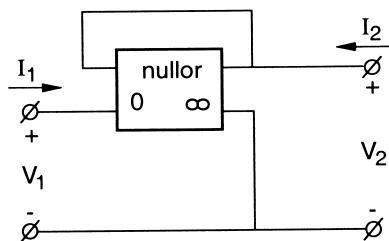


Fig. 1.2.2.a: Voltage follower with a nullor symbol

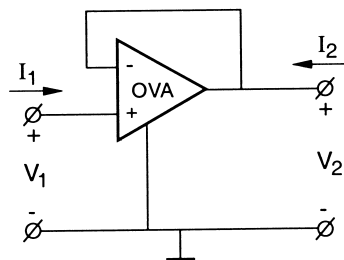


Fig. 1.2.2.b: Voltage follower with an OVA symbol

The voltage follower has the unique property that the voltage amplification factor

$$A_u = V_2/V_1 = 1 \text{ at } I_f = 0 \quad (1.2.2)$$

precisely equals plus unity, independently of any passive components, if the amplifier satisfies the three requirements: high gain, low input offset voltage and current, and a low input bias current. The accuracy of the plus-unity voltage transfer is not limited by the tolerances of any passive components. Note that the accuracy of the minus-unity voltage transfer of a voltage inverter does depend on the tolerance of a ratio of two impedances, as shown in Chapter 3.1, Fig. 3.1.2.

The voltage follower uses the most important attribute of a floating input port, viz. that the potential at one input terminal precisely follows the potential at the other input terminal.

1.3 Operational Current Amplifier (OCA)

A nullor approximation which has only the input port grounded and the output port floating [1.8] will be called an "operational current amplifier" (OCA). An output port with a floating character is difficult to construct, as we will see in Chapter 9. However, this labour is rewarded for applications requiring a high output impedance by using feedback in series coupling with the output port. This series feedback results in an exit with a current-source character, while the grounded input port with parallel feedback assures a low entrance impedance.

Current Amplifier

The most elementary application of the OCA is a current amplifier, whose circuit is shown in Fig. 1.3.1.b with an OCA symbol. The amplifier is the current dualogon of the voltage amplifier of Fig. 1.3.1.a. The amplification factor

$$A_i = -I_2/I_1 = -(Y_1 + Y_2)/Y_1, \text{ at } V_i = 0, \quad (1.3.1)$$

is accurately determined by the admittance ratio $(Y_1 + Y_2)/Y_1$ if the amplifier satisfies: a high gain, a low input offset voltage and current and an output port with a low output bias current, because this current is directly added to the output. Note, that the minus sign merely results from the choice of the opposite current notations of I_1 and I_2 . The low entrance impedance allows current sensing at a low entrance voltage V_i . The current source character at the exit yields an accurate current transfer independently of the load impedance.

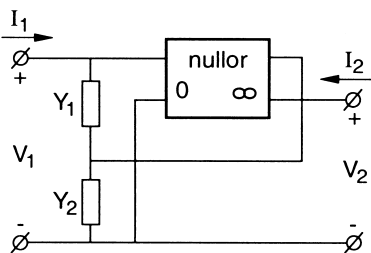


Fig. 1.3.1.a: Current amplifier with a nullor symbol

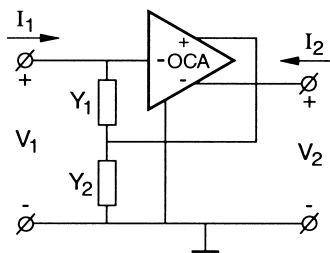


Fig. 1.3.1.b: Current amplifier with an OCA symbol

Current Followers (CF)

A special situation occurs if the negative input terminal of the OCA is connected with the output terminal. We will call such a configuration a "current follower" (CF), because the exit current follows the entrance current. This circuit is the current dualogon of the voltage follower. The circuit is drawn in Fig. 1.3.2.a with a nullor symbol and in Fig. 1.3.2.b with an OCA symbol.

The current follower has the unique attribute that the current amplification factor

$$A_i = -I_2/I_1 = I, \text{ at } V_i = 0, \quad (1.3.2)$$

precisely equals plus unity, independently of any passive component values, if the gain is high, the input offset voltage and current is low, and if the output port has a low bias current. In contrast, the current-amplification factor of a current mirror, which nominally is minus unity, does depend on the matching of two passive elements (see Chap. 3.4).

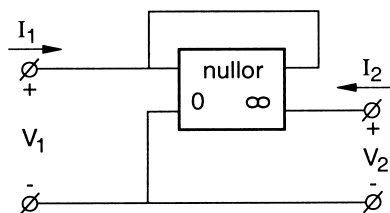


Fig. 1.3.2.a: Current follower with a nullor symbol

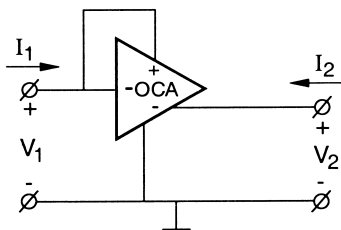


Fig. 1.3.2.b: Current follower with an OCA symbol

Note that the minus sign in Eq. (1.3.2) is needed because the output current I_2 is defined in the opposite direction regarding I_2 , when the current is being transferred through the CF.

The current-follower action reveals the most important attribute of a floating output port, namely that the current which flows into one output terminal is precisely followed by the current which flows out of the other output terminal. This attribute is the very dualogon of the voltage-follower action of a floating input port.

1.4 Operational Floating Amplifier (OFA)

A nullor approximation which has both the input and the output ports floating [1.9] will be called an "operational floating amplifier" (OFA) [1.8, 1.9]. Earlier it was called a "monolithic nullor" [1.10], or second generation current conveyer [1.11]. The construction of such a universal active device combines the demands of both floating input and output

ports.

The OFA provides the maximum freedom for composing feedback configurations. With simple passive components it is possible to apply negative feedback in series with input and output ports, which results in both a high entrance and exit impedance.

Voltage-to-Current Converter

A specific application of the OFA is the voltage-to-current converter or transadmittance amplifier. Such a circuit is shown in Fig. 1.4.1.a with a nullor symbol and in Fig. 1.4.1.b with a practical OFA symbol. The voltage-to-current transfer factor

$$Y_t = I_2/V_1 = Y_1, \text{ at } I_1 = 0, \quad (1.4.1)$$

will be accurately determined by one admittance $-Y_1$ if the amplifier satisfies four requirements: high gain, low input offset voltage and current, low input bias current, and low output bias current. The negative feedback in series with both ports ensures a high entrance impedance and a high exit impedance, which gives the transactor a voltage-sensing entrance and a current-source exit character.

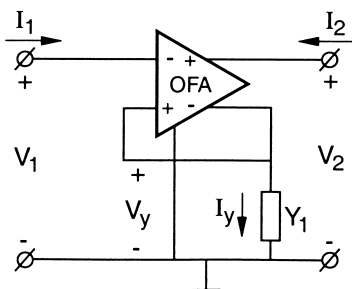
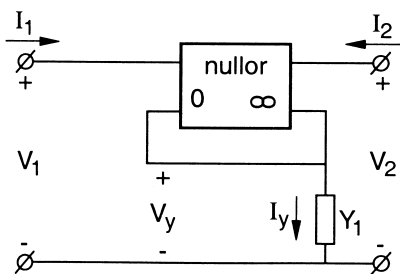


Fig. 1.4.1.a: Transadmittance amplifier with a nullor symbol

Fig. 1.4.1.b: Transadmittance amplifier with an OFA symbol

Voltage and Current Follower (VCF)

In fact, the transadmittance amplifier of Fig. 1.4.1.a/b does not apply all potentialities of the OFA. It is applied in the special case in which the lower terminal of the input port is connected with the lower terminal of the output port. This connection may simplify the construction of the OFA, because no voltage level shifter is needed between the input circuit and one output terminal, as we will see in Chapter 9.2. An OFA with this connection can be called a "voltage and current follower" (VCF).

A nullor which has this connection is also called a "three-terminal nullor" or a "unitor" [1.12]. In Fig. 1.4.1.b the VCF firstly acts like a voltage follower, accurately transferring the entrance voltage V_i towards the voltage V_y on the upper side of the admittance Y_i , and secondly like a

admittance Y_i towards the current I_2 at the upper exit terminal.

1.5 Conclusion

A classification of universal active devices has been given on the basis of the number of ports which are connected to ground or to each other. The more ports not internally connected, the more freedom there is in the choice of the feedback configuration although this creates more complications with the construction of the device. Fig. 1.5.1 presents an